
Group 14	
Joseph Lai Lok Hong	1005216
Teo Zhao Rong Javier	1005033
Aw Yong Jia Min Kellie	1005466
Pung Junhao Louis	1005039
Harikrishnan Chalapathy Anirudh	1005501
Lek Jie Wei	1005007

The structure of the adder that we adopted is a combination of the variable carry select adder, as well as the carry lookahead adder. Within our JSIM file we utilized recursion to create the subcircuits for the G, P and C outputs of each "block", as we noticed a reoccurring pattern of logic devices within our design. Furthermore, buffers were utilized to minimize the load-dependent delays. The diagram of our optimized 32-bit adder is as shown below:

 

Our group chose the **16**<sup>th</sup>-bit output for the CNF, aand the fastest timing that our adder can pass is 3ns, with it being at **2.795ns**.